
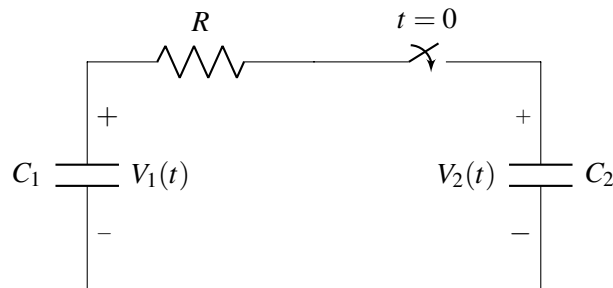


1. Two capacitors

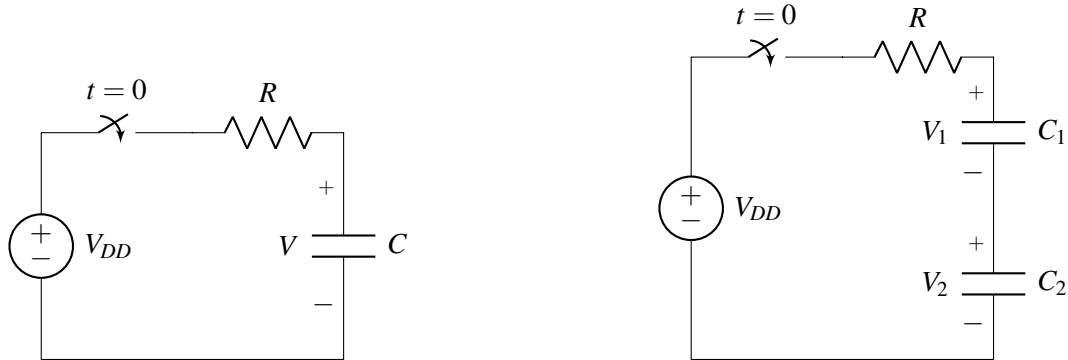


- (a) Using nodal analysis, find the differential equation describing  $V_2(t)$  after the switch closes ( $t \geq 0$ ).
- (b) Assuming  $V_1(0) = 10\text{V}$  and  $V_2(0) = 5\text{V}$ , find the solution to the differential equation found in part (a). Use component values  $C_1 = 1\text{fF}$ ,  $C_2 = 4\text{fF}$ , and  $R = 10\text{k}\Omega$ .
- (c) How does  $V_2(t = \infty)$  compare with what we expect from 16A (charge sharing)?
- (d) Calculate the energy stored in  $C_1$  and  $C_2$  versus time.
- (e) Find the difference in total energy stored in the capacitors at  $t = \infty$  and  $t = 0$ .
- (f) Calculate the energy dissipated by the resistor. Compare it to the difference in the total energy stored in the capacitors at  $t = 0$  and  $t = \infty$ .
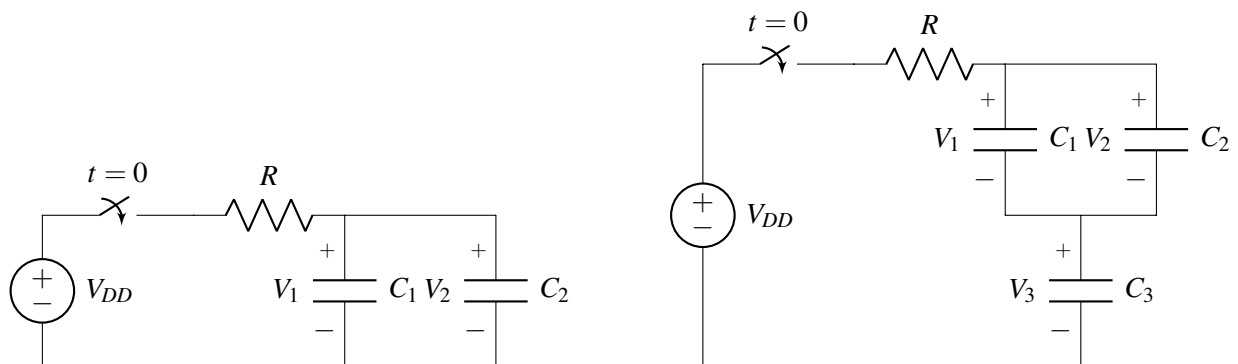
## 2. RC Circuit Variants



Circuit A on left, circuit B on right

- Using nodal analysis, find and solve the differential equation describing  $V$  after the switch closes ( $t \geq 0$ ) in circuit A. Assume the capacitor is initially discharged ( $V(t \leq 0) = 0V$ ).
- Using nodal analysis, find and solve the differential equation describing  $V_1 + V_2$  (the total voltage across the capacitors) after the switch closes ( $t \geq 0$ ) in circuit B. Assume both capacitors are initially discharged ( $V_1(t \leq 0) = V_2(t \leq 0) = 0$ ).



Circuit C on left, circuit D on right

- Using nodal analysis, find and solve the differential equation describing  $V_1$  (the total voltage across the capacitors) after the switch closes ( $t \geq 0$ ) in circuit C. Assume both capacitors are initially discharged ( $V_1(t \leq 0) = V_2(t \leq 0) = 0$ ).
- Using nodal analysis, find and solve the differential equation describing  $V_1 + V_3$  (the total voltage across the capacitors) after the switch closes ( $t \geq 0$ ) in circuit D. Assume all capacitors are initially discharged ( $V_1(t \leq 0) = V_2(t \leq 0) = V_3(t \leq 0) = 0$ ).

### Contributors:

- Kyle Tanghe.
- Jaymo Kang.